


## Appendix A: Transistor Analysis for the FM Transmitter

Reference: *The ARRL Handbook* 73<sup>rd</sup> Edition, 1996 ISBN 0-87259-173-5 pp. 8.24-8.25

The 2N2222A NPN transistor's maximum power  $P_{\max}$  is 0.5 Watts. Power dictates transmission range and exceeding this maximum will overheat and destroy the transistor. Recall that power is calculated as

$$P = I_c V_{ce}$$

Here,  $I_c$  is the transistor collector current and  $V_{ce}$  is the transistor collector and emitter voltage.

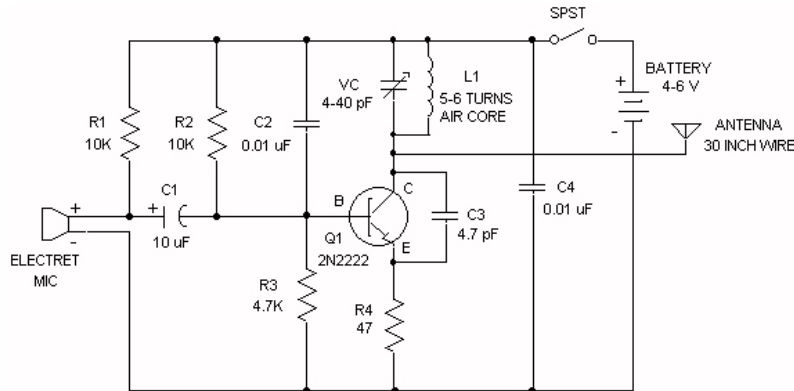

NOTE 1: L1: length = 0.25 inch  
diameter = 0.265 inch  
5 to 6 turns yields approx. 0.17 uH  
NOTE 2: VC set at 12.5 pF yields 108.8 MHz

In the schematic, the collector voltage  $V_c$  is the 6 Volt battery and is related to the emitter voltage  $V_e$  as

$$V_{ce} = V_c - V_e = 6 - V_e$$

Bipolar transistors like the 2N2222A have a 0.7 Volt difference between  $V_e$  and the base voltage  $V_b$

$$V_b - V_e = 0.7 \text{ Volts}$$

The schematic shows that  $V_b$  results from a voltage divider created by the two resistors  $R_2$  and  $R_3$ . Calculating, one has

$$V_b = \frac{6R_3}{R_2 + R_3} = \frac{6 \cdot 4.7 \text{ k}\Omega}{10 + 4.7 \text{ k}\Omega} = 1.92 \text{ Volts}$$

Consequently, the emitter voltage and emitter current become

$$V_e = 1.92 - 0.7 = 1.22 \text{ Volts}$$

$$I_e = \frac{V_e}{R_4} = \frac{1.22 \text{ V}}{47 \text{ }\Omega} = 25.96 \text{ mA}$$

From the schematic, the emitter and collector currents are approximately equal. As such the power now can be calculated. Since  $V_{ce} = 6 - 1.22 = 4.78$  Volts the resulting power of the wireless transmitter is

$$P = I_c V_{ce} = 25.96 \text{ mA} \cdot 4.78 \text{ V} = 124 \text{ mW}$$